 





Frequency Divider (Clock Divider)

ECE-111 Advanced Digital Design Project



Clock

- ❑ Clock is a signal which is repetitive in nature after some period of time
 - In digital circuits, clock is a smallest unit of time when processing happens and sometimes it is also called as a “cycle”
- ❑ Modern digital systems have multiple clocks where each of the core clock vibrates at a specific frequency
 - Clock frequency is typically measured in MHz or GHz
- ❑ Typically, in digital systems multiple clocks with desired frequency are generated using frequency divider from a single reference clock

 

Clock Parameter Definitions

- ❑ **Positive edge** = 0 to 1 transition (also know as **Posedge** or **Rising Edge**)
- ❑ **Negative edge** = 1 to 0 transition (also know as **Negedge** or **Falling edge**)
- ❑ **Positive Level** = Positive edge to Negative edge (also know as **ACTIVE HIGH Level**)
- ❑ **Negative Level** = Negative edge to Positive edge (also know as **ACTIVE LOW Level**)
- ❑ **1 Clock Time Period (T)** = Time between successive transitions in the same direction
 - Positive edge to Positive edge OR Negative edge to Negative edge
- ❑ **Clock Width (t)** = Time during which the value of the clock signal is HIGH or LOW
- ❑ **Frequency** = $1 / \text{Clock Time Period} = 1 / T$
- ❑ **Duty Cycle** = Ratio of clock on time to clock off time (or Ratio of clock width 't' to clock period 'T')

  


What is a Frequency Divider ?

- ❑ A frequency divider, also called a clock divider, is a circuit that takes an input signal of a frequency (f_{in}), and generates an output signal of a scaled down frequency (f_{out})

$$f_{out} = f_{in} \div n, \quad \text{where } n \text{ is an integer}$$

 
- ❑ For power of 2 integer division toggle mode flip-flops are used in a chain as a divide by two counter.
 - One flip-flop will divide the clock, f_{in} by 2, two flip-flops will divide f_{in} by 4 (and so on).
 - This is one of benefit of using toggle flip-flops for frequency division s that the output at any point has an exact 50% duty cycle




Clock Divide by 2

- ❑ Clock divide by 2 can be developed using single D-FlipFlop with inverted output of flipflop connected to input 'D' of flipflop

 - Reference clock (CLK_IN) is connected to flipflop clock pin
- Flipflop output Q produces derived clock (CLK_OUT) which is 1/2 time of CLK_IN time period


 
```
module clock_divide_by_2(  
    input  CLK_IN, reset,  
    output logic CLK_OUT);  
  
    always_ff@(posedge CLK_IN, posedge reset)  
    if (reset)  
        CLK_OUT <= 0;  
    else  
        CLK_OUT <= ~CLK_OUT;  
endmodule: clock_divide_by_4
```



Clock Divide by 4

```
module clock_divide_by_4 #(parameter N = 4)(
  input  clkin, reset,
  output logic clkout);

  logic [$clog2(N)-1:0] cnt_value;
  always_ff@(posedge clkin, posedge reset)
  begin
    if (reset) begin
      cnt_value <= 0;
      clkout <= 0;
    end
    else if(cnt_value == $clog2(N)-1) begin
      cnt_value <= 0;
      clkout <= ~clkout;
    end
    else
      cnt_value <= cnt_value + 1;
    end
  end
endmodule: clock_divide_by_4
```

For N=2, after cnt_value of 0, 1 clk_out value will be flipped from previous value


\$clog2 function returns the ceiling of the logarithm to the base 2.

Example :

for N=4, \$clog2(4) will return 2


for N=6, \$clog2(6) will return 3

For N=8, \$clog2(8) will return 3

 


Question : If parameter N value is changed in SystemVerilog code to value 8, would above mentioned circuit work as divide by 8 ?

Clock Divide by 4 Example

 


**clkout is 4
times slower
than clkin**

 - Freq divide By 2^N
- $N=2 \Rightarrow$ Divide By 4



Let's Design Clock Divide by 3

 

Note: Over a count of 6, we have three full clock cycles and one full out cycle.

Clock Frequency Divide by 3

❑ Can clock divide by 4 implementation code re-used to create clock divide by 3 logic ?


```
module clock_divide_by_3(  
  input logic clkkin, reset,  
  output logic clkout);  
  logic [1:0] cnt_value;  
  always_ff@(posedge clkkin or posedge reset)  
  begin  
    if (reset == 1) begin  
      cnt_value <= 0;  
      clkout <= 0;  
    end  
    else if(cnt_value == 2) begin  
      cnt_value <= 0;  
      clkout <= ~clkout;  
    end  
    else  
      cnt_value <= cnt_value + 1;  
    end  
  end  
endmodule: clock_divide_by_3
```

Would changing cnt_value == 2 (i.e. counting 0,1,2) result in clock divide by 3 ?

Answer : No !


It will behave as clock divide by 6 instead of 3 since cnt_value is incremented at every posedge of clkkin, so clkout will be '1' for 3 clkkin cycles and '0' for 3 clkkin cycles. So 1 clkout == 6 clkkin. See below

 clkout time period
is 6 times than
clkkin time period



Clock Divide by 3 ($F/3$) – Implementation 1

 
□ Clock Frequency divide by 3 using Modulo-3 counter



Clock Divide by 3 (Implementation-1)

```
module clock_divide_by_3(  
    input clkin, reset,  
    output logic clkout);  
  
    logic [1:0] cnt_value;  
    logic count3_done, r_count3_done;  
  
    always_ff@(posedge clkin, posedge reset) begin  
        if (reset) begin  
            cnt_value <= 0;  
        end  
        else begin  
            if(cnt_value == 2) begin  
                ....  
                ....  
            end  
            else begin  
                ....  
                ....  
            end  
        end  
    end  
  
    ...continued
```

 Implement Modulo-3 counter
which does binary count of 0,1,2
and once count value reaches 2,
then set count3_done to = 1 and
count value is reset to '0'



Implement negedge clk
triggered flipflop to register
output of modulo-3 counter
"count3_done"


```
always_ff@(<add sensitivity list, remember negedge clk>) begin  
    if (reset) begin  
        ....  
    end  
    else begin  
        ....  
    end  
end  
assign clkout = (count3_done | r_count3_done);  
endmodule: clock_divide_by_3
```

Clock Divide by 3 (Implementation-2)

❑ Alternate implementation using two counters ?

- One counter for counting posedge of clkin and other counting negedge of clkin
- Whenever either counter reaches a count of '2' (i.e. counts 0,1,2 three edges then generate clkout=1

```
module clock_divide_by_3 (  
    input clkin, reset,  
    output logic clkout);  
  
    // local counter variable  
    logic [1:0] posedge_count, negedge_count;  
  
    // posedge clock counter  
    always_ff@(posedge clkin) begin  
        .....  
        .....  
    end  
    Add Reset condition  
    In Non-reset condition  
    increment posedge_count ?  
  
    // negedge clock counter  
    always_ff@(negedge clkin) begin  
        .....  
        .....  
    end  
    Add Reset condition  
    In Non-reset condition  
    increment negedge_count ?  
  
    // generate divide by 3 clock  
    assign clkout = ((posedge_count == 2) | (negedge_count == 2));  
endmodule: clock_divide_by_3
```

 


Homework Assignment

❑ Develop SystemVerilog RTL model for Clock Divide By $2N+1$ (odd factor)

- Synthesize clock divide by 7 design and run simulation using testbench provided
- Review synthesis results (resource usage and RTL netlist/schematic)
- Review input and output signals in simulation waveform.
- Assume below mentioned primary port names and SystemVerilog RTL module name **clock_divide_by_3**.

❑ Primary Ports for carry_lookahead_adder module

 - Input clkin, reset (Asynchronous active high reset)
- Output clkout



❑ Report should include :

- SystemVerilog design
- Synthesis resource usage and schematic generated from RTL netlist viewer
- Simulation snapshot and explain simulation result to confirm RTL model developed works as clock divide by 7