 


```


# // and may not be used in any way not expressly authorized by SLSW.
# //
# Loading sv_std.std
# Loading work.uart_top_testbench(fast)
# Loading work.uart_top(fast)
# Loading work.uart_tx(fast)
# Loading work.uart_rx(fast)
#
# run -all
# Test Passed - Correct Byte Received time=          3070  expected=a5  actual=a5
# Test Passed - Correct Byte Received time=          6430  expected=a8  actual=a8
# Test Passed - Correct Byte Received time=          9710  expected=ab  actual=ab
# Test Passed - Correct Byte Received time=         12990  expected=ae  actual=ae
# ** Note: $stop      : testbench.sv(96)
#   Time: 13650 ns  Iteration: 0  Instance: /uart_top_testbench
# Break in Module uart_top_testbench at testbench.sv line 96
# Stopped at testbench.sv line 96
# exit
# End time: 15:40:14 on Mar 09,2026, Elapsed time: 0:00:01
# Errors: 0, Warnings: 0
End time: 15:40:14 on Mar 09,2026, Elapsed time: 0:00:02
*** Summary *****
      qrun: Errors:  0, Warnings:  0
      vlog: Errors:  0, Warnings:  0
      vopt: Errors:  0, Warnings:  1
      vsim: Errors:  0, Warnings:  0
      Totals: Errors:  0, Warnings:  1
Finding VCD file...
./dump.vcd

```

The tests passed when testing with the given testbench



 ve opening in a new browser window, set that option on your profile page.



Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

We can see the clocks syncing and the done signal being sent shortly after the signal has been received. This shows a successful communication between the modules.

In this simulation we can also see the Baud Rate and Oversampling Accuracy working as minted along with the state transitions and the verification of the data packets that we receive.

Current State	Input / Condition	Next State	Moore Output (tx)
IDLE	tx_start == 0	IDLE	1 (Marking)
IDLE	tx_start == 1	START	1
START	s_tick count < 15	START	0 (Start Bit)
START	s_tick count == 15	DATA	0

DATA	s_tick count < 15 OR bit_cnt < 7	DATA	data_buffer[bit_cnt]
DATA	s_tick count == 15 AND bit_cnt == 7	STOP	data_buffer[7]
STOP	s_tick count < 15	STOP	1 (Stop Bit)
STOP	s_tick count == 15	IDLE	1 (Triggers tx_done_tick)
Current State	Input / Condition	Next State	Moore Output (rx)
IDLE	rx == 1	IDLE	0
IDLE	rx == 0 (Start edge)	START	0
START	s_tick count < 7	START	0
START	s_tick count == 7	DATA	0 (Sample middle of Start)
DATA	s_tick count < 15 OR bit_cnt < 7	DATA	0
DATA	s_tick count == 15 AND bit_cnt == 7	STOP	0 (Sample middle of Bit 7)
STOP	s_tick count < 15	STOP	0
STOP	s_tick count == 15	IDLE	1 (Data complete)

Code (rx):

```
// UART RX RTL Code
```

```

module uart_rx #(parameter NUM_CLKS_PER_BIT=16)
(input logic clk, rstn,
input logic rx, // input serial incoming data
output logic done, // indicates 8-bit serial data is converted into 8-bit parallel data and available on dout port
output logic [7:0] dout // 8-bit parallel data output
);

// count variable
logic [$clog2(NUM_CLKS_PER_BIT)-1:0] count;

// state encoding and state variable
enum logic[3:0]{
    RX_IDLE      = 4'b0000,
    RX_START_BIT = 4'b0001,
    RX_DATA_BIT0 = 4'b0010,
    RX_DATA_BIT1 = 4'b0011,
    RX_DATA_BIT2 = 4'b0100,
    RX_DATA_BIT3 = 4'b0101,
    RX_DATA_BIT4 = 4'b0110,
    RX_DATA_BIT5 = 4'b0111,
    RX_DATA_BIT6 = 4'b1000,
    RX_DATA_BIT7 = 4'b1001,
    RX_STOP_BIT  = 4'b1010} state;

// FSM with single always block for next state,
// present state flipflop and output logic
always_ff@(posedge clk) begin
    if(!rstn) begin
        done <= 0;
        count <= 0;
        dout <= 0;
        state <= RX_IDLE;
    end
    else begin
        case(state)
            RX_IDLE: begin
                done <= 0;
                count <= 0;
                dout <= 0;
                // Wait for rx = 0 indicating start bit
                if(rx == 0) state <= RX_START_BIT;
                else state <= RX_IDLE;
            end
            RX_START_BIT: begin
                // sample start bit value at mid-point, for start bit counter
                // value = 7 is midpoint
                // wait for rx to transition from 1 to 0
                if(rx == 0 && count == ((NUM_CLKS_PER_BIT-1)/2)) begin
                    done <= 0;
                    state <= RX_DATA_BIT0;
                    count <= 0;
                    dout <= 0;
                end else begin
                    count <= count + 1;
                end
            end
            RX_DATA_BIT0: begin
                // sample start bit value at mid-point
                // for each databit to get midpoint count value is 16
                // counting starts from midpoint of previous bit and ends at midpoint
                // of current data bit

```

```

        if(count == (NUM_CLKS_PER_BIT-1)) begin
            dout[0] <= rx;
            count <= 0;
            state <= RX_DATA_BIT1;
        end else begin
            count <= count + 1;
        end
    end
end

```

```

RX_DATA_BIT1: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[1] <= rx;
        count <= 0;
        state <= RX_DATA_BIT2;
    end else begin
        count <= count + 1;
    end
end
end

```

```

RX_DATA_BIT2: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[2] <= rx;
        count <= 0;
        state <= RX_DATA_BIT3;
    end else begin
        count <= count + 1;
    end
end
end

```

```

RX_DATA_BIT3: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[3] <= rx;
        count <= 0;
        state <= RX_DATA_BIT4;
    end else begin
        count <= count + 1;
    end
end
end

```

```

RX_DATA_BIT4: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[4] <= rx;
        count <= 0;
        state <= RX_DATA_BIT5;
    end else begin
        count <= count + 1;
    end
end
end

```

```

RX_DATA_BIT5: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[5] <= rx;
        count <= 0;
        state <= RX_DATA_BIT6;
    end else begin
        count <= count + 1;
    end
end
end

```

```

RX_DATA_BIT6: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[6] <= rx;
    end
end

```

```




        count <= 0;
        state <= RX_DATA_BIT7;
    end else begin
        count <= count + 1;
    end
end

RX_DATA_BIT7: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        dout[7] <= rx;
        count <= 0;
        state <= RX_STOP_BIT;
    end else begin
        count <= count + 1;
    end
end

RX_STOP_BIT: begin
    if(count == (NUM_CLKS_PER_BIT-1)) begin
        done <= 1;
        state <= RX_IDLE;
        count <= 0;
    end else begin
        count <= count + 1;
    end
end

endcase
end
end
endmodule: uart_rx

```

   

	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	38
2		
3	▼ Combinational ALUT usage for logic	54
1	-- 7 input functions	3
2	-- 6 input functions	18
3	-- 5 input functions	12
4	-- 4 input functions	13
5	-- <=3 input functions	8
4		
5	Dedicated logic registers	38
6		
7	I/O pins	23
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	rx_...put
12	Maximum fan-out	24
13	Total fan-out	385
14	Average fan-out	2.79

Shows the

logic registers and the ALUT logic used as well as pins and total logic utilization

